

PHASE- AND DELAY-LOCKED LOOP CLOCK CONTROL IN DIGITAL SYSTEMS

Zeljko Zilic


- Clock distribution problem in synchronous systems
 - Jitter and clock skew
- Use of Phase-Locked Loops (PLLs) and Delay-Locked Loops (DLLs) in digital systems
- PLL/DLL building elements for digital designers
- Dynamic clock management issues

PLLs/DLLs: WHY BOTHER?

- No need to use PLLs in digital systems on chip ~5 years ago
- Recent increase in digital logic speed and level of integration
 - Communication applications need PLLs/DLLs
- Synchronous circuit speed: degraded by clock skew
 - Clock cycles of 10ns (100 MHz) cannot tolerate few ns of clock skew
- PLLs introduce closed-loop timing compensation, as opposed to open-loop clock skew reduction mechanisms
 - Clock tree distributions and skew tolerance schemes are open-loop schemes that can reduce, but not eliminate skew

CLOSED-LOOP SKEW COMPENSATION

 
- Clock skew is measured and compensated by a control loop
 - Sources outside the loop are uncompensated
- Typical situation: loop around the buffer



- Inserts negative delay!

PHASE- AND DELAY-LOCKED LOOPS

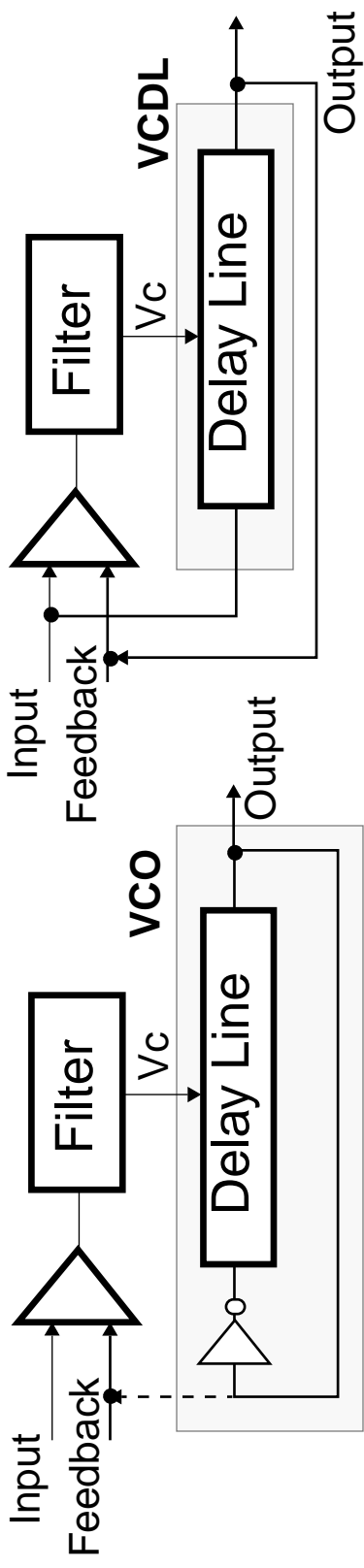- Two closed-loop skew control mechanisms
- Both circuits align input clock with selected feedback signal



Phase-Locked Loop


Delay-Locked Loop

- Voltage controlled ring oscillator (VCO) vs. voltage controlled delay line (VCDL)


- Control voltage: V_c

PLLS IN FREQUENCY SYNTHESIS

- Dividing clock rate

 

- Multiplying clock rate

 


VOLTAGE CONTROLLED OSCILLATORS

- Core of the PLLs/DLLs - oscillators that can be controlled by voltage (or current)
 - Ideally, frequency is proportional to control voltage
- Our application: square wave is usually obtained by a delay line acting as a ring oscillator
 - Ring with odd number of inverters
- Good VCOs must have the following
 - Low intrinsic jitter
 - High power supply noise rejection ratio

DELAY ADJUSTMENT RANGE

❑ Cannot have both large range of delays and fine-grain adjustments

 
❑ Current-starved vs. capacitor-loaded delay line




❑ Delay line with N delay elements has N taps. By allowing each tap to be used, the range is extended

SUPPLY NOISE REJECTION

- Noise rejection of CMOS inverters

 

 
- Supply sensitivity of current-starved inverter delay line




REDUCING POWER SUPPLY NOISE

□ Improve the power supply

• Passive: Low-pass filter

 


• Active: Linear regulated power supply

 


LIVING WITH POWER SUPPLY NOISE

 - ❑ Use differential delay elements
- ❑ Differential inverter chain
- ❑ Or, the following circuit:




PHASE COMPARATORS


□ XOR Based

 

□ Sequential

 


PHASE FREQUENCY DETECTOR

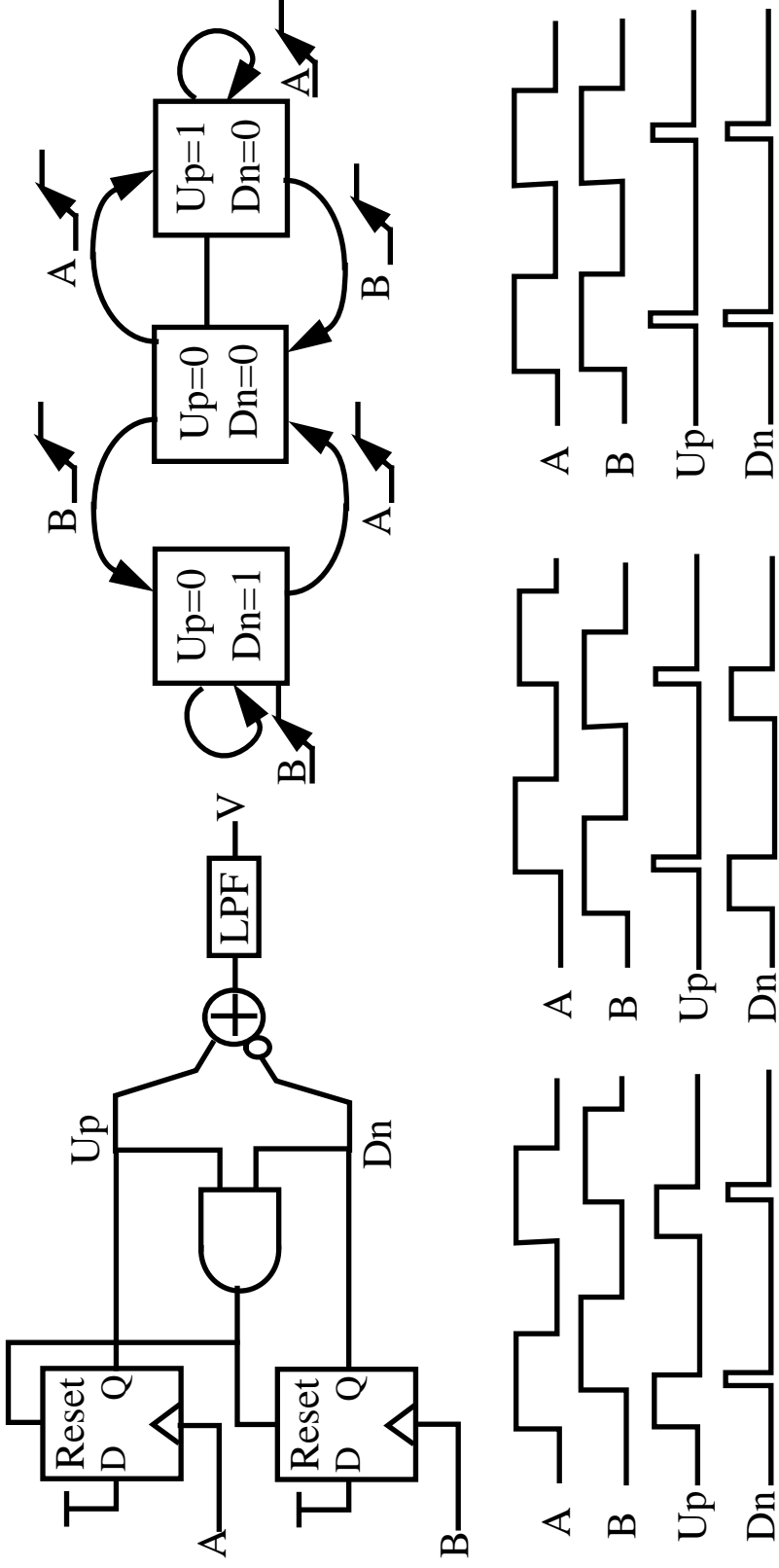


LOOP FILTERS

 - Function: controlling the loop dynamics
 - Removes high-frequency (noise), stabilizes the response
- Passive filters: RC network



- Active filter:

 


$$L(s) = \frac{(sR_2C + 1)}{sR_1C}$$

Osc. Frequency ω_1 and dumping factor

$$\omega_1 = \sqrt{\frac{K_{PD}K_{VCO}}{RC}}, \quad \zeta = \omega_1 \frac{R_2C}{2}$$

CHARGE PUMP PLLS

□ Typical Implementation

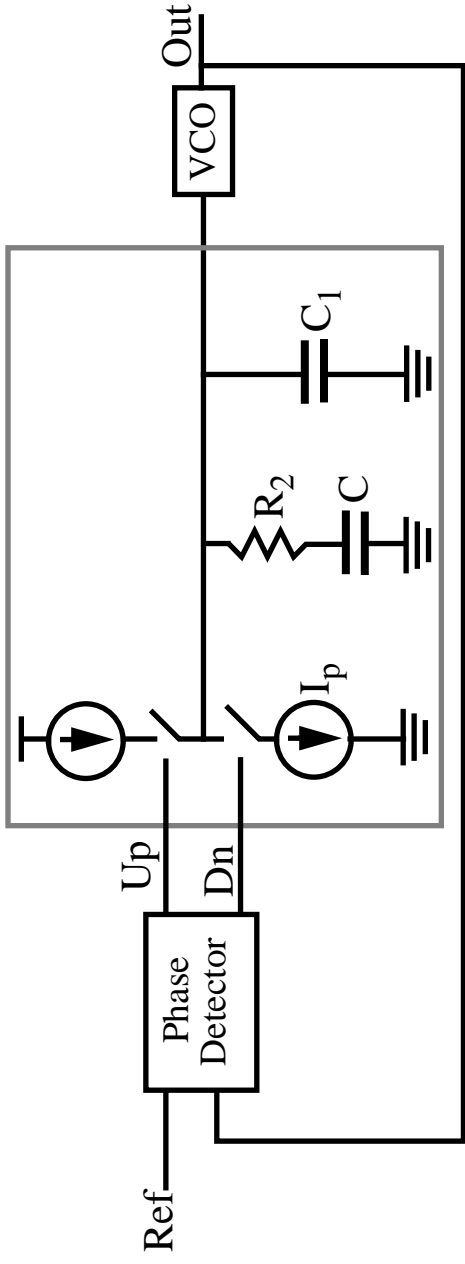

□ Loop stability: comparable to active filter


- Want: high osc. frequency ω_1 . (Rule of thumb: 1/10 of reference clock.)

DLL IMPLEMENTATIONS

- DLLs stability simpler to analyze: first order systems
 - First order loop filters suffice
- However, many complications:
- *False lock* problem: DLL loop delay is not T , but one of: $0T$, $2T$, ... nT , ...
 - Resolving problem: (digital) circuits that disable false lock
- “Turbo” mode: allows fast acquisition by more current in charge-pump
- Bang-Bang Controller: high-gain detectors with rapid capture, but small clock phase excursions

CLOCK MANAGER EXAMPLE

ORCA FPGA Programmable Clock Manager

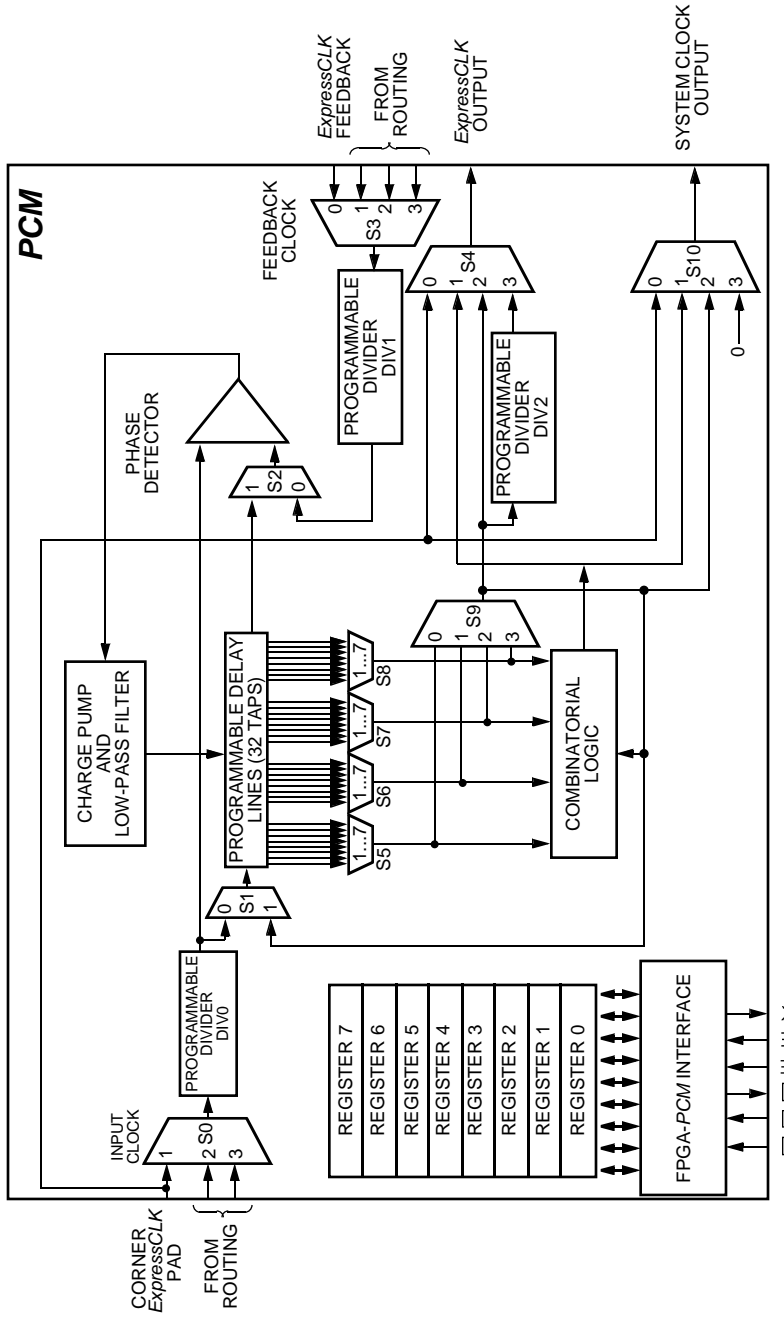

CLOCK MANAGER USE

- PLL mode: close delay line ring
- PLL frequency multiplication by M: divide feedback by M
- PLL frequency multiplication by M/N: above plus N in output divider
- DLL mode: delay line fed by input
- DLL programmable delay: select tap X as output
- DLL duty cycle adjustment: select tap X as to duty cycle circuit
- DLL clock multiplication/duty cycle adjustment: select tap X and tap $16+X$ as inputs to clock doubler

DYNAMIC CLOCK MANAGEMENT

- Low power applications: run as fast as needed, no faster
 - Impossible with current clock managers
- Dynamic clock management problems:
 - Clock dividers work incorrectly
 - Oscillations in forbidden states
 - Transient behaviors
 - VCOs work inefficiently, need external programming
 - PLLs might not achieve locking range
 - Need external intervention to adjust VCO length
 - Transient behaviors
 - Slow response
- Solutions: Patented Dynamic Clock Divider, PLL